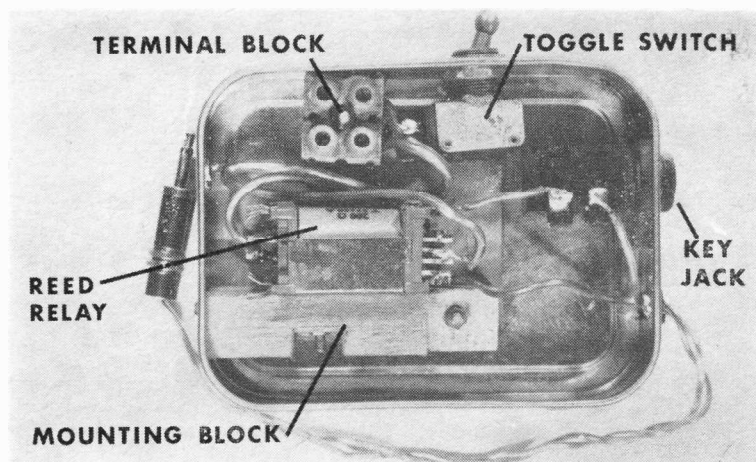


The unit as constructed by G6AB and described in his article.



carrying the stabilised HT supply to the output socket—is then cut. The two wires under the chassis which are terminated in the twin terminal block under the PSU chassis are in turn connected to the two cut ends. In the author's case the wire which was cut was the blue insulated one, though this may not apply to all these PSU's.

Netting


It will now be observed that the cutting of this wire has destroyed the netting facilities previously available, and that is the reason for the single-pole toggle switch in the tobacco tin. This is joined up across the twin terminal box in the add-on unit, and when put in the closed position, will restore HT supplies to the oscillator if the "Net, Standby, Transmit" switch is put to "Transmit," enabling netting to be done without putting the carrier on the air.

Construction

The circuit diagram shows the connections to the components and the photograph can be used as a guide to the layout. The original keying jack plug, the coil of the relay, and the extra jack socket are wired in series, which puts the 200-ohm coil of the relay in the cathode circuit of the PA when the key is closed.

Break-in working can now be easily accomplished by providing a separate aerial for the receiver and keying the AT5 through the add-on unit, though at G6AB the transmitter aerial is used as this is changed over from "receive" to "send" by another relay, operated by an additional contact on the key.

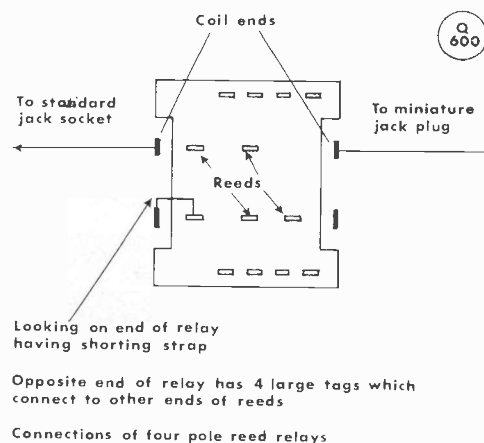The relay used here has actually got four separate normally-open gold-plated contacts, vacuum sealed in a glass tube, inside the 200-ohm coil. When the coil is energised by the cathode current of the PA valve all four contacts close. If the constructor wishes, all four reeds



can be strapped in parallel to share the load (though each one is rated to carry 500 mA!). Alternatively, one of the reeds can be used to apply an earth to the station receiver when the key is closed, in which case it is recommended that the two-pole terminal block in the add-on unit be replaced by a four-pole and the extra pair of wires run to the aerial and earth terminals of the receiver.

Operation

In conclusion, for the benefit of CW operators who have not yet used break-in, it is most satisfying to be able to monitor one's own transmission and at the same time to listen between the dots and dashes and hear immediately if any QRM should appear on the channel, or if the station with whom one is in contact has any difficulty in receiving one's signal. He can stop your transmission at any time by just pressing his key or sending a string of dots. Break-in thus leads to better operating.