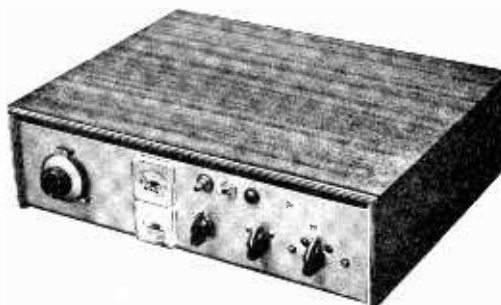


# The 'WYVERN' 160 Metre Solid State Transmitter



— Part 2.

by

John R. Green, B.sc., G3WVR

The second article in our 3-part series which describes the construction of a comprehensive transmitter design incorporating semiconductors throughout.

IN LAST MONTH'S ISSUE THE OVERALL DESIGN OF THE transmitter was described as also, in detail, were the v.f.o., the wideband driver section and the doubler and driver stage. This month's article covers the power amplifier stage and the power supply. The concluding article, to be published next month, will deal with the modulator, VU meter driver and general assembly and testing.

## POWER AMPLIFIER

The circuit diagram for the p.a. stage is given in Fig. 11. This diagram also includes the power switching around S1(a) to S1(e).

The heart of the stage is the BD123 transistor, which has been chosen for three reasons:

- (a) the frequency response cut-off  $f_T$ , of 85MHz gives a more than adequate performance at 2MHz,
- (b) the power dissipation capacity of 45W gives a safeguard against overheating and damage,
- (c) the VCE (collector-emitter maximum voltage) of 60 volts gives a reasonable safety margin since on modulation peaks the collector to emitter instantaneous voltage (peak) can be as much as four times the normal supply voltage, i.e. 48 volts.

304

The drive to the base of the BD123 is controlled by RV1, which is mounted on the front panel of the transmitter. TR7 is pulsed on by positive-going r.f. half-cycles. The consequent pulses of collector current passing through the 2 turn winding of L4 are shaped by the 20 turn tuning winding before radiation. Both windings are close-wound, direct on the rod using 20 to 24 s.w.g. enamelled wire.

Loading and tuning adjustments for the p.a. are as for a conventional valve transmitter, with the exception that the loading setting is far less critical, particularly if the aerial is not quarter wave resonant, and final loading adjustments are carried out by means of the drive potentiometer.

It is important to note that all drive components, i.e. RV1, L2 tuning and L3 tuning, are normally set for maximum p.a. current; whereas the p.a. tuning is adjusted for minimum p.a. current.

Always begin tuning operations with RV1 turned up only sufficiently to draw, say, 500mA of current through the p.a. meter, and then perform initial tuning and loading. Gradually increase the drive given by RV1 until the legal maximum (830mA at 12 volts) is achieved, then make final fine tuning adjustments. Failure to follow this procedure could cost an output transistor (about £1).

RADIO & ELECTRONICS CONSTRUCTOR

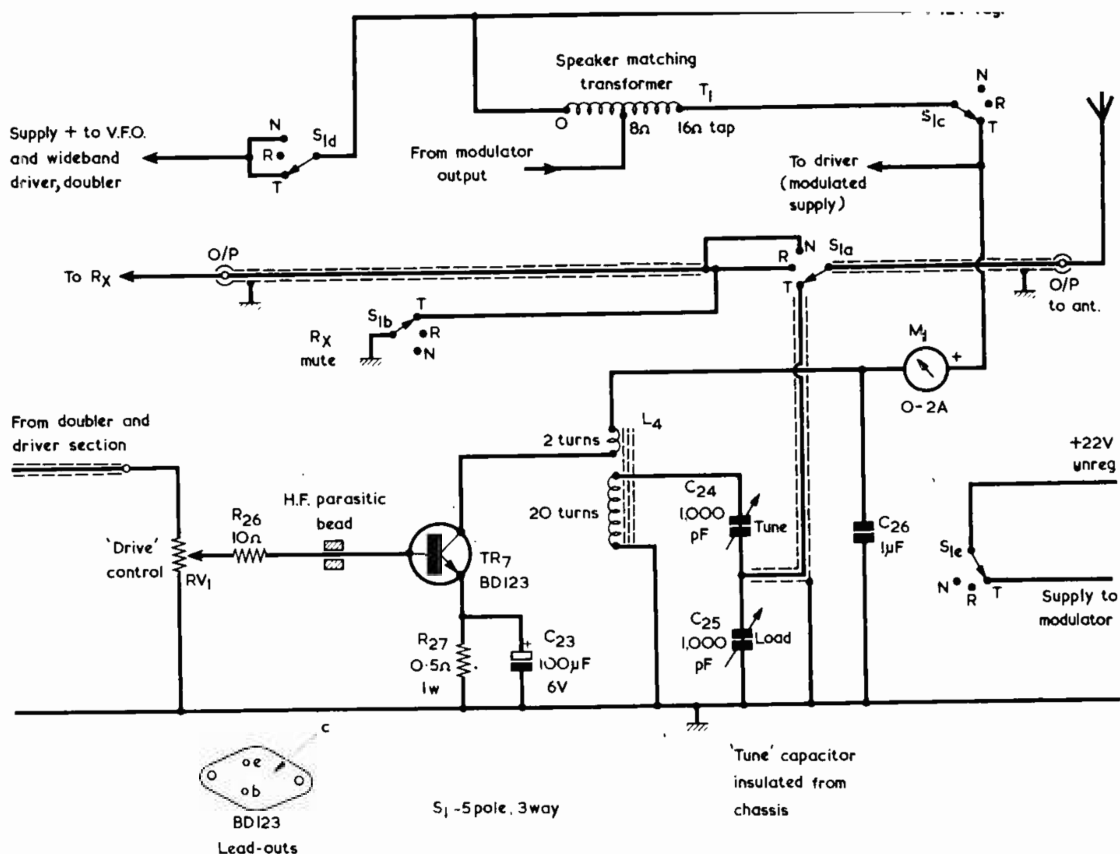


Fig. 11. The p.a. stage. Shown also are the Net, Receive and Transmit switching circuits and the modulation transformer, T<sub>1</sub>

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{2}$  watt 10%, unless otherwise stated)

R <sub>26</sub>	10Ω
R <sub>27</sub>	0.5Ω 1 watt
R <sub>28</sub>	1kΩ
R <sub>29</sub>	22kΩ
R <sub>30</sub>	1kΩ
R <sub>31</sub>	1kΩ
R <sub>32</sub>	220Ω
R <sub>33</sub>	0.25Ω 1 watt, see text
RV <sub>1</sub>	500Ω potentiometer, wire-wound

### Capacitors

C <sub>23</sub>	100μF electrolytic, 6 V.Wkg.
C <sub>24</sub>	1,000pF variable
C <sub>25</sub>	1,000pF variable
C <sub>26</sub>	1μF plastic foil
C <sub>27</sub>	1,000μF electrolytic, 25 V.Wkg.
C <sub>28</sub>	2,000μF electrolytic, 25 V.Wkg.
C <sub>29</sub>	100μF electrolytic, 25 V.Wkg.

### Inductors

T <sub>1</sub>	Speaker matching transformer, 8Ω and 16Ω or 8Ω and 15Ω, minimum rating 10 watts
T <sub>2</sub>	Mains transformer, secondary 0-12-15-20-24-30 volts at 2 amps, Douglas type MT3AT
L <sub>4</sub>	P.A. output coil, wound on ferrite rod 6ins. by $\frac{1}{2}$ in. diameter

### Semiconductors

TR7	BD123
TR8	BFY50/2N3053
TR9	2N3053
TR10	2N3250/2N3905/2N3702
TR11	2N3055
D1-D4	Silicon rectifiers, 2A 100 P.I.V.
ZD2, 3	6.8V 200mW zener diodes

### Switches

S <sub>1</sub>	5-pole 3-way, wafer
S <sub>2</sub>	s.p.s.t. toggle

### Meter

M <sub>1</sub>	0-2A meter
----------------	------------

### Neon

NE1	Panel-mounting neon assembly with integral series resistor
-----	--

### Fuses

F1-3	2 amp anti-surge, with holders
------	--------------------------------

### Miscellaneous

Ferrite lead	
2 coaxial sockets	
4-way tagstrip	
3 pointer knobs	
Printed circuit board	
16 s.w.g. aluminium	
Coaxial cable	

The ferrite rod, on which is wound the output coil, is clearly visible here. The component to the left of the rod is the modulation transformer

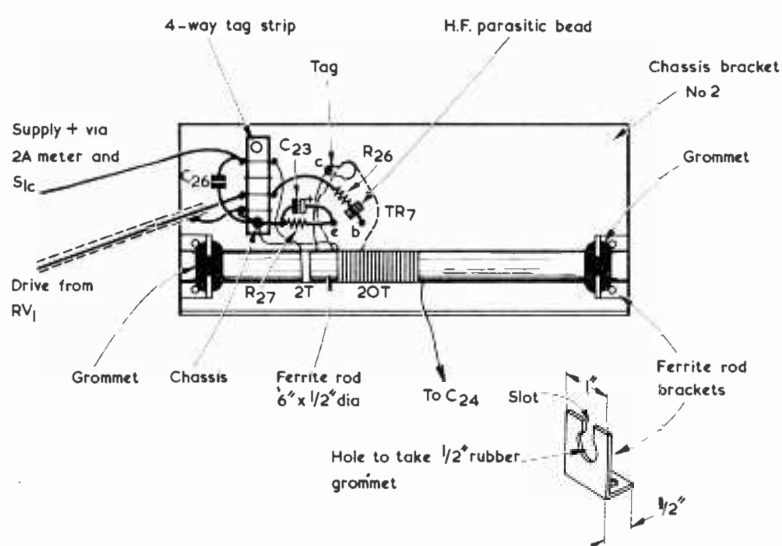
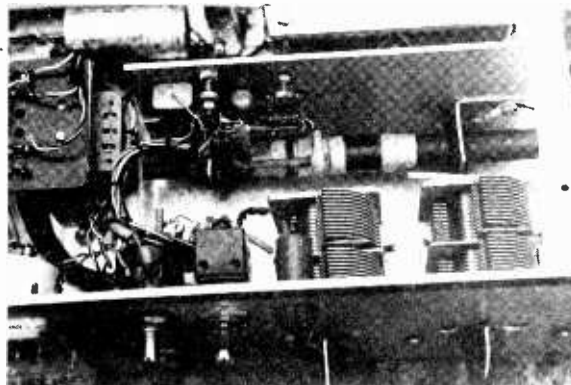


Fig. 12. Physical layout of the p.a. stage. The parts are mounted on Chassis Bracket No 2


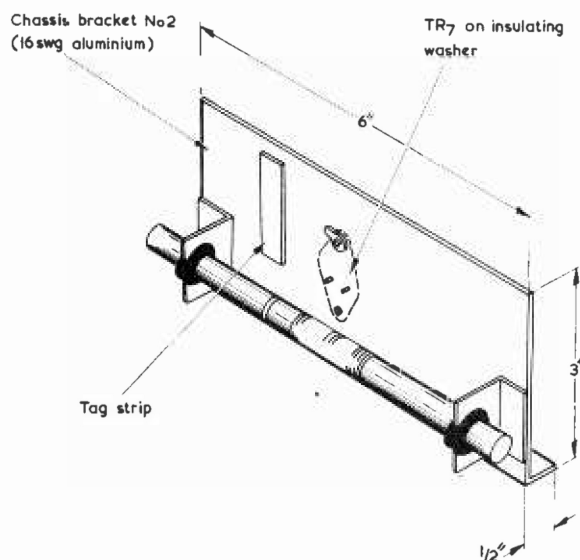


Fig. 13. Details of the Chassis Bracket No 2

Also, do not use a smaller ferrite rod for L4 or saturation of the ferrite may result, destroying the transformer action. If desired, use a larger ferrite rod but *do* ensure that it is suitable for operation at 2MHz, as many ferrite grades are not. The rod used by the author is 6ins. long by  $\frac{1}{2}$ in. diameter, and was obtained from G. W. Smith & Co. (Radio) Ltd., 3 Lisle St., London, W.C.2.

Fig. 11 also shows the switching carried out by S1(a) to (e). This is quite simple and straightforward and the circuits controlled at each switch position can be readily traced through. The modulation transformer T1 is a speaker matching transformer having taps at  $8\Omega$  and  $16\Omega$ . A transformer having taps at  $8\Omega$  and  $15\Omega$  could alternatively be employed if this should prove easier to obtain. Whatever transformer is employed *must* have a power capability of at least 10 watts audio handling.

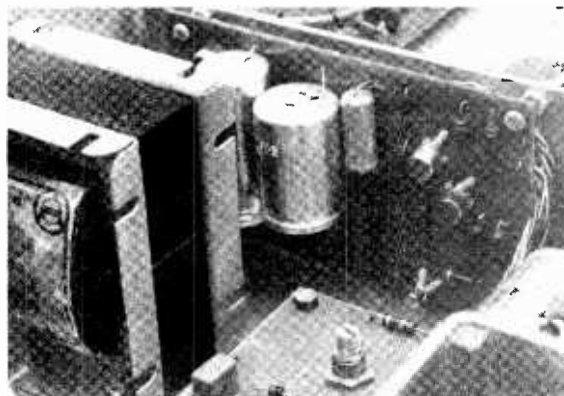As will be illustrated in greater detail in next month's article, in which the general assembly will be dealt



*A view of the power supply board. This is partly obscured by the mains transformer*

The modulation transformer, T1, is positioned between the v.f.o. box and Chassis Bracket No. 2.

## POWER SUPPLY

The circuit diagram of the power supply is shown in Fig. 14. The design incorporates the simplest form of regulation for the 12 volt supply, using zener diodes

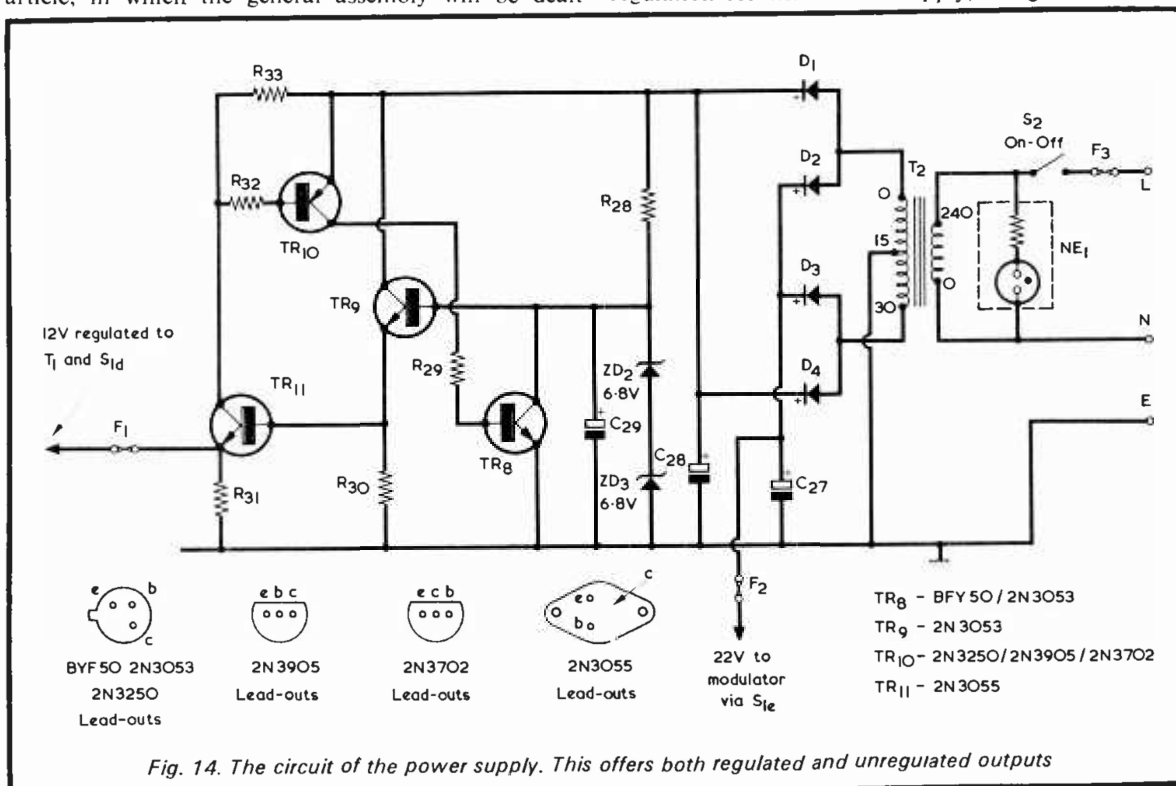


Fig. 14. The circuit of the power supply. This offers both regulated and unregulated outputs



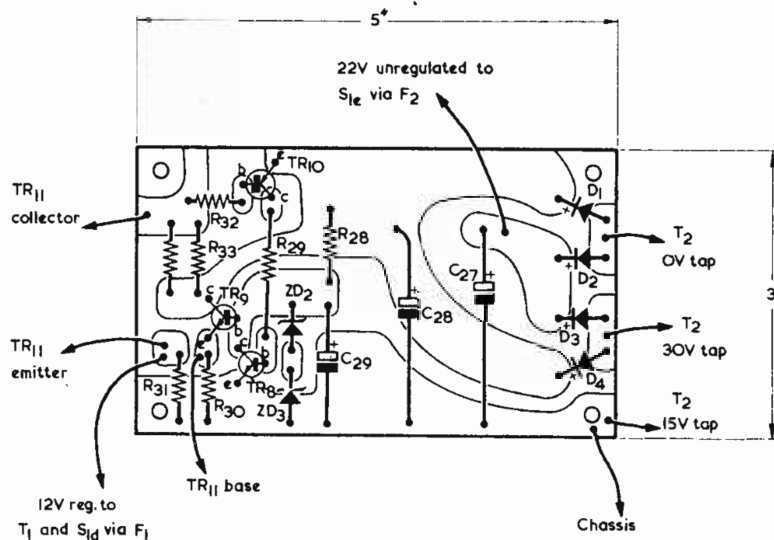


Fig. 15. The power supply printed circuit board, as seen from the component side.

ZD2 and ZD3 and the emitter followers TR9 and TR11. Overload protection is given by TR10 and TR8. If the current drawn through R33 causes a voltage to appear across it which is sufficiently high to allow base current to flow in TR10, this transistor becomes conductive. Its collector current flows in the base

circuit of TR8, whereupon TR8 causes a reduction in the voltage across ZD2 and ZD3 and, in consequence, in the regulated output. The current limit is 2.5 amps.

A 22 volt unregulated supply is also provided for the Class B modulator.

The mains transformer, T2, has a number of secondary windings, of which only the 0, 15 and 30 volt windings are employed here. The 15 volt winding becomes the earthed centre-tap in this arrangement.

The use of fuses in the mains input and regulated and unregulated output circuits is recommended, and they can be located in any available space in the transmitter. A neon mains indicator lamp with integral series resistor may be fitted, if desired.

The printed circuit board for the power supply is reproduced, full size, in Fig. 15. The view is from the component side of the board. In the prototype R33 is made up of two  $\frac{1}{2}$  watt  $0.5\Omega$  resistors in parallel and two resistors are shown, in Fig. 15, in the R33 position. The board is mounted, with spacing stand-off washers to Chassis Bracket No. 3, which is illustrated in Fig. 16. The bracket also acts as a heat sink for TR11, the body of which is on the opposite side of the bracket to the board. TR11 is insulated from the bracket by a mica washer and insulated mounting bushes.

The whole power supply (both 12 and 22 volt outputs) may be replaced by a car battery or other 12 volt accumulator (but *not* by dry batteries, which cannot supply the current required). The author's transmitter incorporates additional sockets and switching to achieve this. It should be pointed out, however, that when running from a 12 volt supply the modulator will not supply the output required for 100% modulation. Incidentally, the 22 volt output from the mains power supply will, of course, drop in voltage under load but this is not detrimental to the modulation quality unless excessive bass frequencies are present.

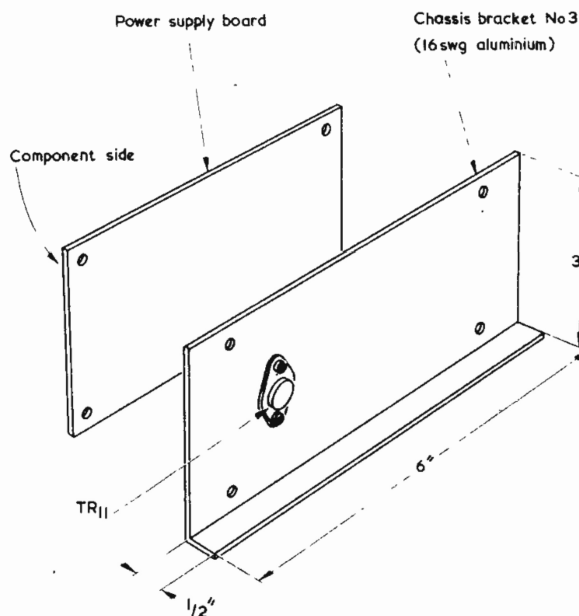


Fig. 16. Fitting the power supply board to Chassis Bracket No 3